

CHAPTER 1**Basic DC Terminology**

Introduction	1-1
The Electric Circuit	1-1
Current (I).....	1-2
Electromotive Force (EMF)	1-3
Potential Difference (PD)	1-3
Voltage (V).....	1-3
Resistance (R)	1-4
Connecting Resistances in Series or Parallel in a DC Circuit	1-5
Ohm's Law	1-7
Loads	1-7
Kirchhoff's Laws	1-7
Electric Power (P)	1-8
Electrical Work	1-9
Electric Unit Prefixes	1-9
Typical Circuit Symbols	1-9

CHAPTER 2**Electrical Components**

Introduction	2-1
Electric Systems	2-1
Electric Circuit Faults	2-2
Busbars	2-3
Protection Devices	2-4
Reverse Current Circuit Breaker (RCCB).....	2-6
Switches	2-6
Electric Generator	2-10
Alternator	2-10
Electric Motor	2-10

CHAPTER 3**Aircraft Batteries**

Introduction	3-1
Lead Acid Battery	3-2
Alkaline Battery (Nickel-Cadmium)	3-3
Battery Venting	3-4
Electrolyte Spillage	3-5
Battery Capacity	3-5
Battery Charging	3-6
Thermal Runaway	3-6
Battery State of Charge	3-6
Battery Condition Check	3-7
Emergency Use	3-7
Connection of Batteries	3-7
Spare Batteries	3-8
Battery Compartment Inspection	3-8

CHAPTER 4**Magnetism**

Introduction	4-1
Magnetism	4-2
Fundamental Laws of Magnetism	4-2
Characteristics of Lines of Magnetic Flux.....	4-3
Classification of Magnetic Materials	4-5
Magnetic Flux	4-5
Flux Density	4-5
Reluctance	4-5
Permeability	4-5
Hysteresis	4-6
Saturation	4-7
Magnetism Produced by Current Flow	4-7
The Electromagnet	4-10
The Relay	4-12
Electromagnetic Induction	4-12

CHAPTER 5**DC Generator Systems**

Introduction	5-1
Generator Systems	5-1
Basic Generator Theory	5-1
A Simple Generator	5-2
Conversion of AC to DC	5-3
DC Generator System Architecture	5-5
DC Generator Construction	5-5
Principle of Operation of a DC Generator	5-6
Types of DC Generator	5-6
Voltage Regulator	5-8
Cut-Out	5-9
Reverse Current Circuit Breaker	5-10
Busbars	5-10
Power Failure Warning	5-11
Ground Power	5-11
DC Generator System Fault Protection	5-12
Twin-Engine DC Electrical System	5-13
Operation of DC Generators in Parallel	5-14
DC Load Sharing	5-14
Operation of an Equalising Circuit	5-15
Single-Engine Aircraft DC Electrical System	5-15
Operation of the Alternator	5-16

CHAPTER 6**DC Motors**

Introduction	6-1
Motors	6-1
The Motor Principle	6-1
DC Motors	6-2
Back EMF	6-3
Direction of Rotation	6-3
Types of DC Motor	6-4
Motor Speed Control	6-6
Actuators	6-8
Split-Field Series Motor	6-9
Electromagnetic Brakes	6-10
Clutches	6-10
Instrument Motors	6-10
Architecture of a Starter/Generator System	6-11
Operation of a Starter/Generator System	6-11
Inverters	6-14
Multiple Inverter Installations	6-15

CHAPTER 7**Inductance and Capacitance**

Introduction	7-1
Inductance	7-1
Self Induction	7-2
Inductors	7-2
Time Constant of an Inductor	7-3
Inductors in Series and Parallel	7-4
Capacitance	7-5
Factors Affecting Capacitance	7-5
Types of Capacitor	7-6
The Charging of a Capacitor	7-7
Discharging of a Capacitor	7-8
The Time Constant of a Capacitor	7-8
Capacitors in Series and Parallel in a DC Circuit	7-9

CHAPTER 8**Basic AC Theory**

Introduction	8-1
Alternating Current	8-1
Advantages of AC Over DC	8-1
Generating AC	8-1
Simple AC Generator	8-2
AC Terminology	8-3
Phasor Representation	8-6

CHAPTER 9**Single Phase AC Circuits**

Introduction	9-1
Single Phase AC Circuits	9-1
The Effect of AC on a Purely Resistive Circuit	9-1
Power in an AC Resistive Circuit	9-1
The Effect of AC on a Purely Inductive Circuit	9-2
Power in an AC Inductive Circuit	9-3
Inductive Reactance (XL)	9-3
The Effect of AC on a Purely Capacitive Circuit	9-4
Power in an AC Capacitive Circuit	9-4
Capacitive Reactance	9-5
Relationship Between Voltage and Current in Capacitive and Inductive AC Circuits	9-5
Resistive and Inductive (RL) Series AC Circuit	9-5
Resistive and Capacitive (RC) Series AC Circuit	9-6
Phase Shift	9-6
Resistive, Inductive, and Capacitive (RLC) Series AC Circuits	9-6
Impedance (Z) in a Resistive, Inductive, and Capacitive (RLC) Series AC Circuit	9-7
Resistive, Inductive, and Capacitive (RLC) Parallel AC Circuit	9-7
Impedance (Z) in a Resistive, Inductive, and Capacitive (RLC) Parallel AC Circuit	9-7
Power in a Resistive, Inductive, and Capacitive (RLC) AC Circuit	9-8
Power Factor	9-9
AC Series Circuit Example	9-9
AC Parallel Circuit Example	9-11

CHAPTER 10**Resonant AC Circuits**

Introduction	10-1
Resonant Circuit.....	10-1
Series Resonant Circuit	10-1
Q Factor in a Series Resonant Circuit	10-3
Parallel Resonant Circuit (Tank Circuit)	10-3
Q Factor in a Parallel Resonant Circuit	10-5
Self Resonance of Coils	10-5
Use of Resonant Circuits	10-5
Tuning Circuits	10-7

CHAPTER 11**Transformers**

Introduction	11-1
Transformers.....	11-1
Construction and Operation	11-1
Types of Transformers	11-3
Transformer Rectifier Units	11-5

CHAPTER 12**AC Power Generation**

Introduction	12-1
Power Generation	12-1
Simple Three Phase Generator	12-1
Star Connection	12-2
Delta Connection	12-3
Advantages of Three Phase Over Single Phase AC Generators	12-4
Voltage and Frequency of AC Generators	12-4
Phase Rotation	12-4
Faults on Three-Phase AC Generators	12-4
Generator Real and Reactive Load Sharing	12-5
Types of AC Generator	12-6
Brushless Three Phase AC Generator	12-7
Constant Speed Drive Unit	12-9
Operation of the Hydro-Mechanical CSDU	12-11
Protection of the Hydro-Mechanical CSDU	12-11
Integrated Drive Generator	12-13
Variable Speed Constant Frequency Power Systems	12-13
Auxiliary Power Unit	12-14
Emergency Ram Air Turbine	12-15

CHAPTER 13**AC Power Generation Systems**

Introduction	13-1
A Typical Frequency-Wild AC System Architecture	13-1
Operation of a Typical Frequency-Wild AC System	13-2
Fault Protection in a Typical Frequency-Wild AC System	13-2
The Constant Frequency Split Busbar AC System	13-4
Operation of a Constant Frequency Split Busbar AC System	13-4
Regulation and Protection of Constant Frequency Units	13-5
Faults on a Constant Frequency Split Busbar AC Generator System	13-5
Emergency Supplies	13-7
Battery Charger	13-7
Battery Power	13-7
Ground Handling Bus	13-7
Constant Frequency Parallel AC System	13-8
Operation of a Constant Frequency Parallel AC System	13-8
Reactive Load Sharing	13-11
Real Load Sharing	13-11
Paralleling	13-12
Fault Protections in a Constant Frequency AC Parallel System	13-12
DC Power Supplies	13-14

CHAPTER 14**AC Motors**

Introduction	14-1
Alternating Current Motors	14-1
Stator-Produced Rotating Magnetic Field	14-1
Induction (Squirrel Cage) Motor	14-2
Two-Phase Induction Motor	14-4
Split-Phase Motor	14-4
The Synchronous Motor	14-5

CHAPTER 15**Semiconductor Devices**

Introduction	15-1
Semiconductor Devices	15-1
Advantages and Disadvantages	15-1
Construction of a Semiconductor	15-1
Doping	15-2
P-Type Material	15-2
N-Type Material	15-3
P-N Junction Diode	15-4
Use of Diodes	15-6
Zener Diode	15-6
Variable Capacitance (VARICAP) Diode.....	15-7
Bi-Polar Transistors	15-7
Operation of a PNP Bi-Polar Transistor	15-8
Operation of a NPN Bi-Polar Transistor	15-9
Disadvantages of Diodes and Transistors	15-9
Transistor Applications	15-10
Integrated Circuits	15-11
The Advantages and Disadvantages of Integrated Circuits	15-11
Types of Integrated Circuits	15-11

CHAPTER 16**Logic Circuits**

Introduction	16-1
Logic Circuits.....	16-1
Number Systems	16-1
Binary Representation	16-2
Basic Logic Gates	16-2
Adder and Subtractor Circuits	16-4
Digital Latch and Flip-Flop Circuits	16-6

CHAPTER 17**Computer Technology**

Introduction	17-1
Computers	17-1
Analogue Computers	17-1
Digital Computers	17-1
Computer Architecture	17-3
Input Devices	17-3
Central Processing Unit	17-4
Output Devices	17-5
Storage Devices	17-5
Operating Systems	17-5
Programming	17-5

CHAPTER 18**HF and Satellite Airborne Communications**

Introduction	18-1
Airborne Communications	18-2
Long Range Communications (Up to 4000 Km)	18-2
Short Range Communications (Up to 450 Km)	18-3
Selective Calling (SELCAL) System	18-4
Satellite Communications (SATCOM)	18-5
Satellite Aircom (SITA).....	18-7